

Electronic Devices & Circuits I 2EI4

Project 4

Instructors: Dr. Haddara

Ashviya Jeyaseelan

As a future member of the engineering profession, the student is responsible for performing the required work in an honest manner, without plagiarism and cheating. Submitting this work with my name and student number is a statement and understanding that this work is my own and adheres to the Academic Integrity Policy of McMaster University and the Code of Conduct of the Professional Engineers of Ontario.

1. Circuit Design


i. XOR Truth Table

A	B	$F = A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

ii. XOR Function


Using DeMorgan's theorem, the function can be determined where: $F = A \oplus B = AB' + A'B = ((AB')' + (A'B)')' = ((A' + B)(A + B'))' = (A'B' + AB)'$

iii. Circuit Schematic

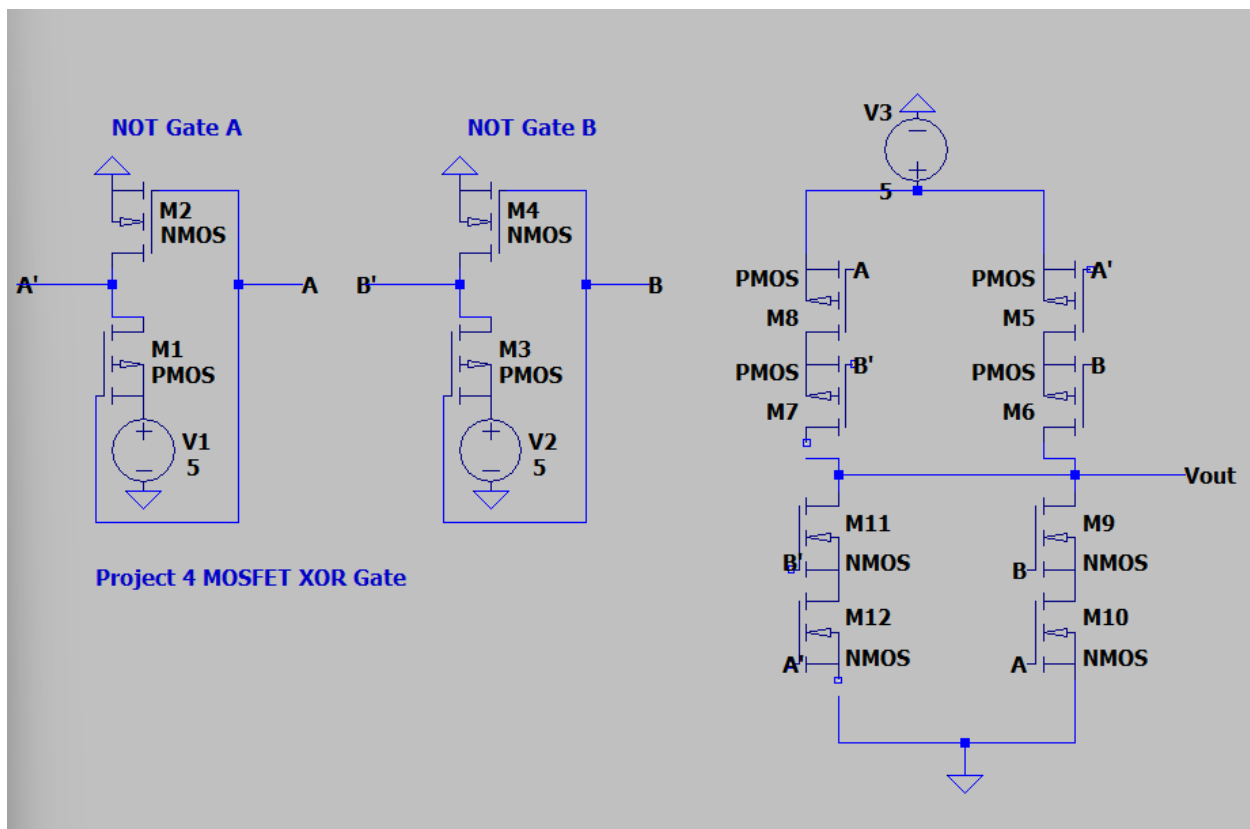

2. Idea Sizing

i. Ideal Ratio

 


ii. Real Sizing

The ideal sizing can be implemented in the hardware design given the assumption that the n-type MOSFETs have $\left(\frac{W}{L}\right) = \frac{2}{1}$ and the p-type MOSFETs have $\left(\frac{W}{L}\right) = \frac{5}{1}$ where the longest path is from VDD to GND, resulting in the sizing ratio of 2.5 equal to that of the ideal scenario. This qualitatively has no impact on the performance, especially since symmetrical inverters are used in the circuit.

3. Testing


i. Circuit Implementation

 

ii. Functional Testing


The result of the functional testing corresponds to the truth table for a XOR, as shown in the table below:

DIO0	DIO1	DIO2
0	0	0
0	1	1
1	0	1
1	1	0

 


 iii. Static Level Testing


The static level testing demonstrates that the MOSFET XOR gate takes the input (C1) and inverses the output (C2), as shown in the AD2 measurements below.



 The first waveform was generated with input A as a square wave between 0V and 5V and input B as 5V, where $V_H = 5.0847$ V and $V_L = -67.22889$ mV.



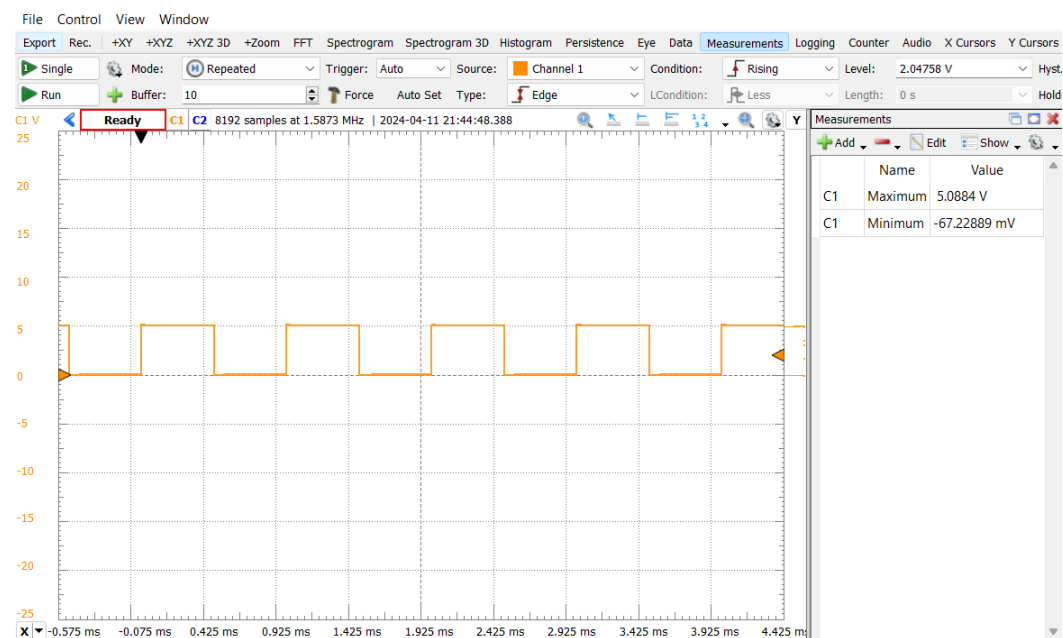
The second waveform was generated with input A as 5V and input B as a square wave between 0V and 5V, where $V_H = 5.0884$ V and $V_L = -67.22889$ mV.



Based on these results, it is evident that the values remain the same with minor variation.


4. Testing



i. Circuit Implementation

 

 ii. Rise and Fall Times

A capacitance load of 100nF was used to produce the waveform, as shown below.



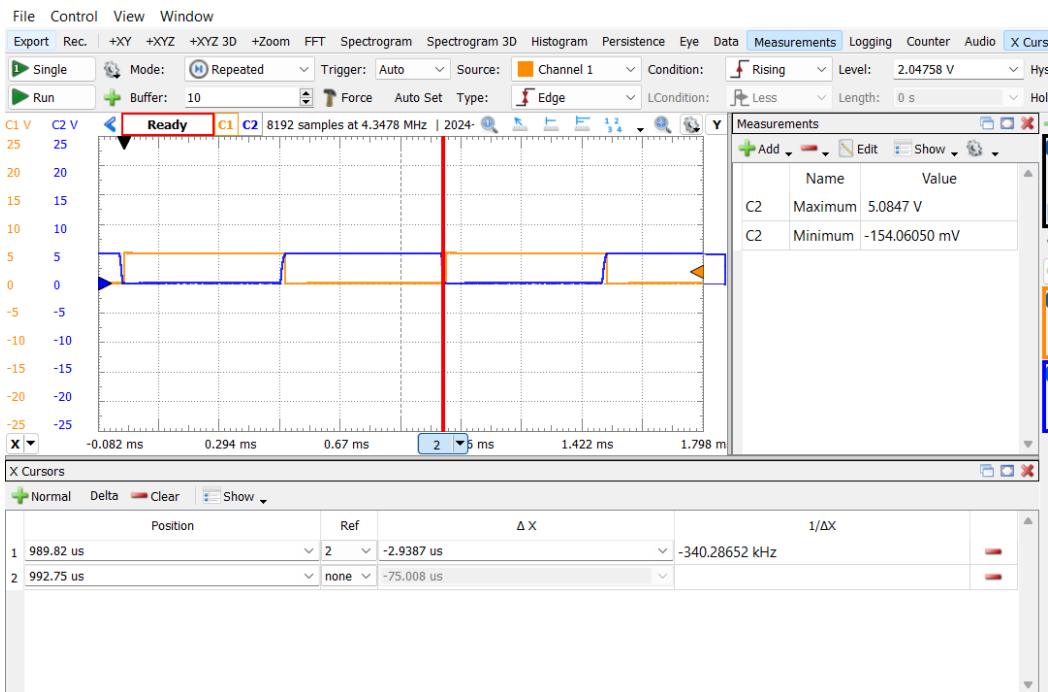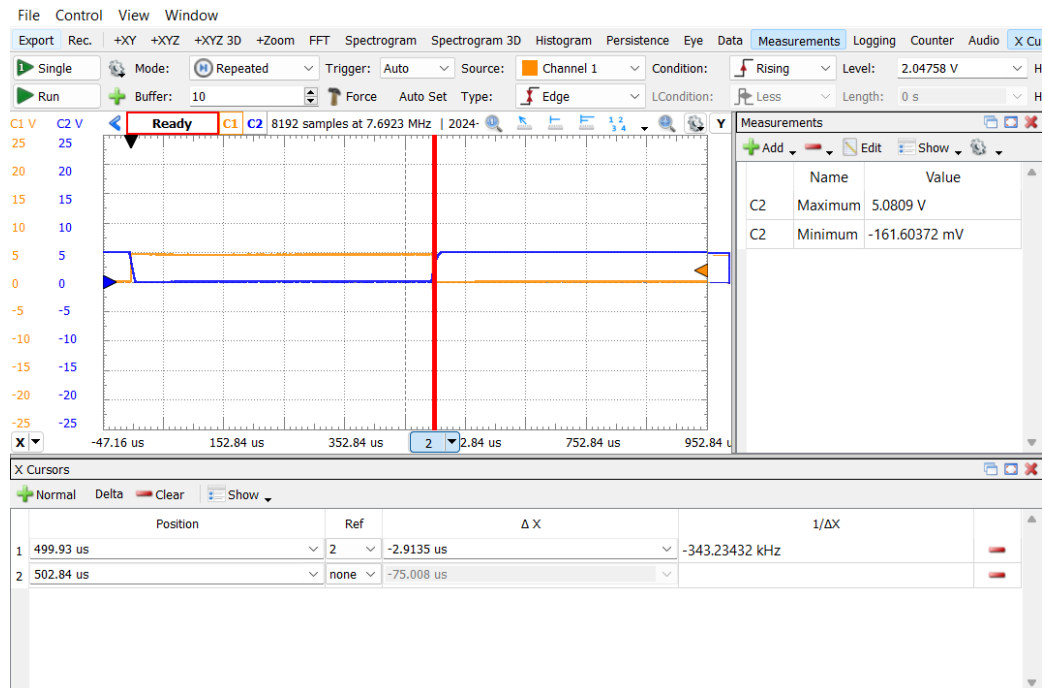

Based on the AD2 measurements, the rising and falling times were determined by taking the difference between the maximum and minimum values of the waveforms. The rising time was 2.9135 us and the falling time was 2.9387 us.

iii. τ_{PLH} , τ_{PHL} , τ_P

According to the AD2 waveforms, the t_{PHL} can be determined by finding the time where the input reaches its maximum and XOR gate reaches 50% of its range, which was 183.87 us. The t_{PLH} can be determined by finding the time where the input reaches its minimum and XOR gate reaches 50% of its range, which was 153.48 us. t_P can then be calculated by taking the average where $t_P = (t_{PHL} + t_{PLH}) / 2 = 168.66$ us.

References

- [1] “CD4007CN Datasheet (PDF) – Fairchild Semiconductor,” *AllDatasheet*. Available: <https://pdf1.alldatasheet.com/datasheet-pdf/view/50834/FAIRCHILD/CD4007CN.html>. [Accessed April 10, 2024].